 



More on Sequential Logic

CS 64: Computer Organization and Design Logic
Lecture #15
Winter 2019

Ziad Matni, Ph.D.
Dept. of Computer Science, UCSB



I'm a CS major

 


What's a CS major?



It means he's afraid
of hardware



No it doesn't

 

CIRCUITS, CPUs,
EMBEDDED SYSTEMS



Stop it Patrick you're
scaring him!

Administrative

- Lab #7
 - Due next week on Wednesday 3/6
 - Paper copy to submit in HFH 2nd Floor (CS64 box)

Administrative

- The Last 3 Weeks of CS 64:


Date	L #	Topic	Lab	Lab Due
2/26	14	Combinatorial Logic, Sequential Logic 1	7 (CL+SL)	Wed. 3/6
2/28	15	Sequential Logic 2		
3/5	16	FSM 1	8 (FSM)	Wed. 3/13
3/7	17	FSM 2		
3/12	18	Digital Logic Review	9 (Ethics)	Fri. 3/15
3/14	19	CS Ethics & Impact Final Exam Review		

Lecture Outline

- More on Sequential Logic
- Class exercises

The Gated D Latch

 
- The gated D-Latch is very commonly used in electronic circuits in computer hardware, especially as a register because it's a circuit that holds memory!



Whatever data you present to the input D,
the D-Latch will **hold** that value (*as long as input E is 0*)
You can **present** this value to output Q *as soon as input E is 1.*

Enabling the Latch Synchronously: The Clocked D Latch

- If you apply a **synchronous clock** on input E, you get a **clocked D latch**.
- A clock is an input that cycles from 1 to 0, then back to 1 again in a set time period
 - e.g.: if a clock input cycles this in a period of 1 ms, we call it a 1 MHz clock (1 Hz = 1 / 1 second)
- **Note 1:** When CLK is 0, both S and R inputs to the latch are 0 too, so the Q output holds its value whatever it is ($Q = Q_0$)

 


- **Note 2:** When CLK is 1:
if $D = 1$, then $Q = 1$,
if $D = 0$, then $Q = 0$

Truth table



D	CK	Q
0	1	0
1	1	1
X	0	Q_0

Clocked D Latch as Digital Sampler

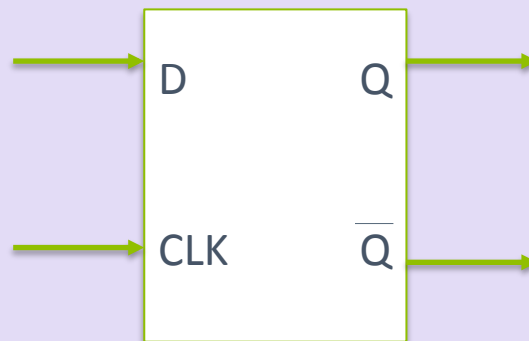
- This clocked latch can be used as a “programmable” memory device that “samples” an input on a regular basis





The Clocked D Latch By Any Other Name...

  

- Observing input and output “waveforms”

 

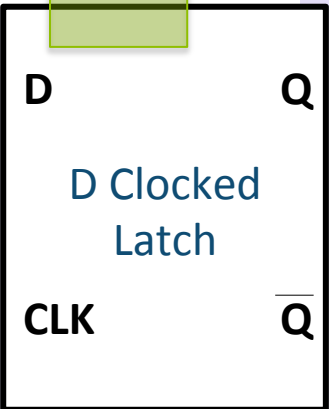 

The Joys of Sampling...


- Sampling data in a periodic way is advantageous
 - I can start designing more complex circuits that can help me do *synchronous* logical functions
 - *Synchronous*: in-time
- Very useful in *pipelining* designs used in CPUs
 - Pipelining: a technique that allows CPUs to execute instructions more efficiently – in parallel

Instr. No.	Pipeline Stage						
	IF	ID	EX	MEM	WB		
1	IF	ID	EX	MEM	WB		
2		IF	ID	EX	MEM	WB	
3			IF	ID	EX	MEM	WB
4				IF	ID	EX	MEM
5					IF	ID	EX
Clock Cycle	1	2	3	4	5	6	7

Instruction fetch, decode, execute, memory access, register write

The Most Efficient Way to Sample Inputs

 
- Instead of sampling the input to the latch using a *level* of the clock...
 - That is, when the clock is “1” (or “0”)





- ... sample the input at the *edge* of the clock
 - That is, when the clock is transitioning from $0 \rightarrow 1$, called a *rising* or *positive* edge
(or it could be done from $1 \rightarrow 0$,
the *falling* edge a.k.a *negative* edge)
 - Why??

The D-FF

 
- When the input clock edge is *rising*, the input (D) is *captured* and placed on the output (Q)
 - Rising edge a.k.a positive edge FF
 - Some FF are negative edge FF (capture on the falling edge)



  

Latches vs. FFs


 
- Latches capture data on an entire 1 or 0 of the clock
- FFs capture data on the edge of the clock
 - This example shows the positive (0→1) edge used




An Improvement on the Latch: The D Flip-Flop

Don't worry about the circuit implementation details, but understand the use!

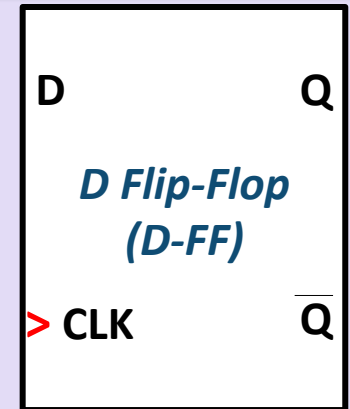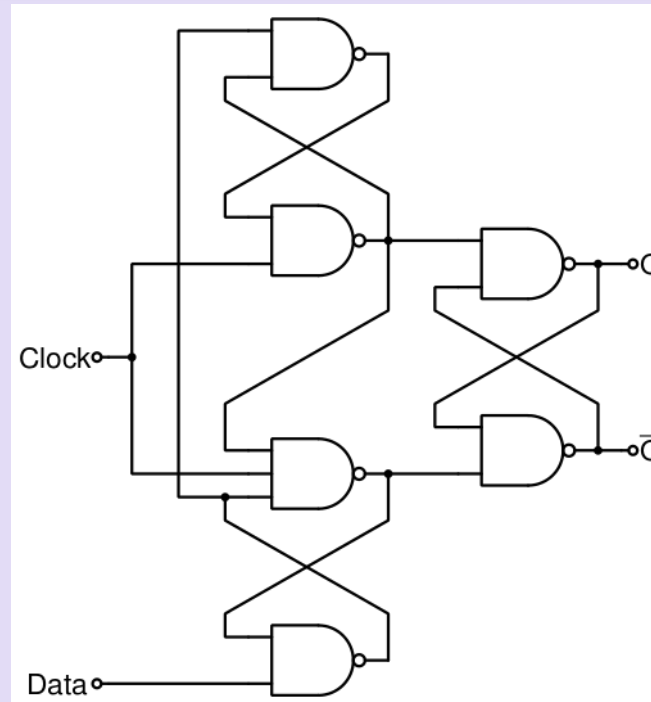The **D Flip-Flop** only changes the output (Q) into the input (D) at the **positive edge** (the 0 → 1 transition) of the clock



As opposed to:

 


Note the (slight) difference in the 2 symbols...


Again, don't worry about the circuit implementation details, but understand the uses!

Popular Uses for D-FFs

- Counter

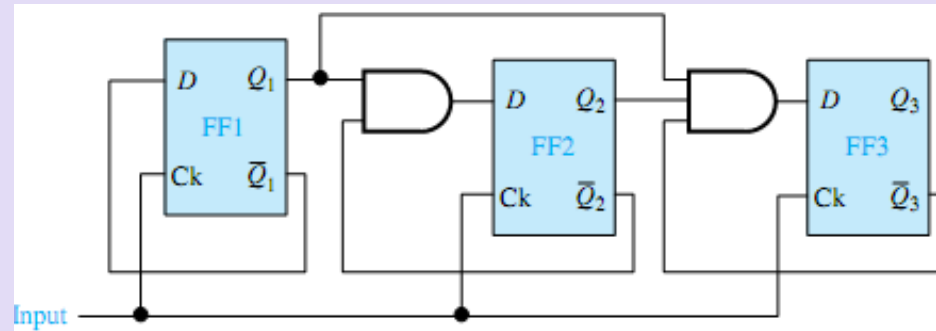


- Serial-to-Parallel converter

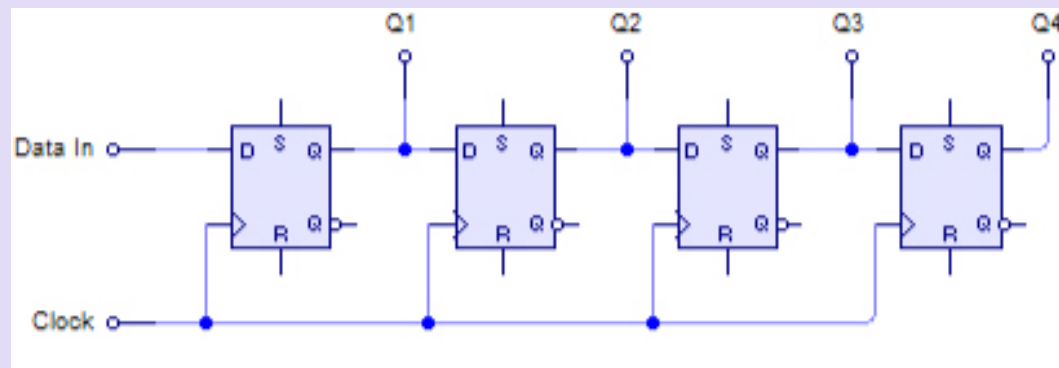


Class Exercise 1

 The figure below shows an RS latch made out of NAND gates (rather than NOR gates). How do Q and \bar{Q} depend on the RS inputs? i.e. verify that the circuit can indeed be used as a RS latch.



Class Exercise 2

 Given waveforms for A, B, C, and Clk (see blackboard), determine the output waveform for F





Class Exercise 3

- Let's design a 3-bit counter using D-FFs and logic gates.
- What's needed:
 - This counts $000 \rightarrow 001 \rightarrow 010 \rightarrow \dots \rightarrow 111 \rightarrow 000$
 - i.e. from 0 to 7 and then loops again to 0, etc...
- To describe this behavior, let's start with a T.T.
 - We'll utilize K-Maps, if needed to figure out what the "next states" look like based on "current states"
 - We'll translate that into a digital circuit design


Solutions to Class Exercises 2 and 3 From Lecture 14

© Ziad Matni, 2018

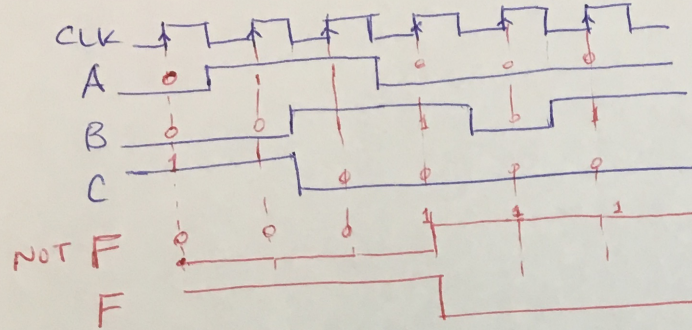 


	Current state			Next state		
	Q ₂	Q ₁	Q ₀	Q ₂ [*]	Q ₁ [*]	Q ₀ [*]
0	0	0	0	0	0	1
1	0	0	1	0	1	0
2	0	1	0	0	1	1
3	0	1	1	1	0	0
4	1	0	0	1	0	1
5	1	0	1	1	1	0
6	1	1	0	1	1	1
7	1	1	1	0	0	0

K-Map for Q₂^{*}

 


$$Q_2^* = Q_2 \cdot \overline{Q_0} + Q_2 \cdot \overline{Q_1} + \overline{Q_2} \cdot Q_1 \cdot Q_0$$

for Q₁^{*}

 


$$Q_1^* = Q_1 \cdot \overline{Q_0} + \overline{Q_1} \cdot Q_0 = Q_1 \oplus Q_0$$

for Q₀^{*}

 

$$Q_0^* = \overline{Q_0}$$

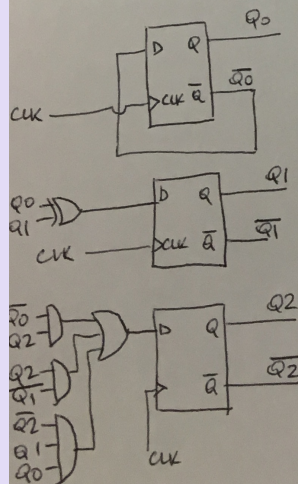

YOUR TO-DOs

- Lab 7
 - Due back on Wednesday
 - Paper copy – not electronic
 - Drop off in the CS64 BOX in HFH 2nd Floor

</LECTURE>